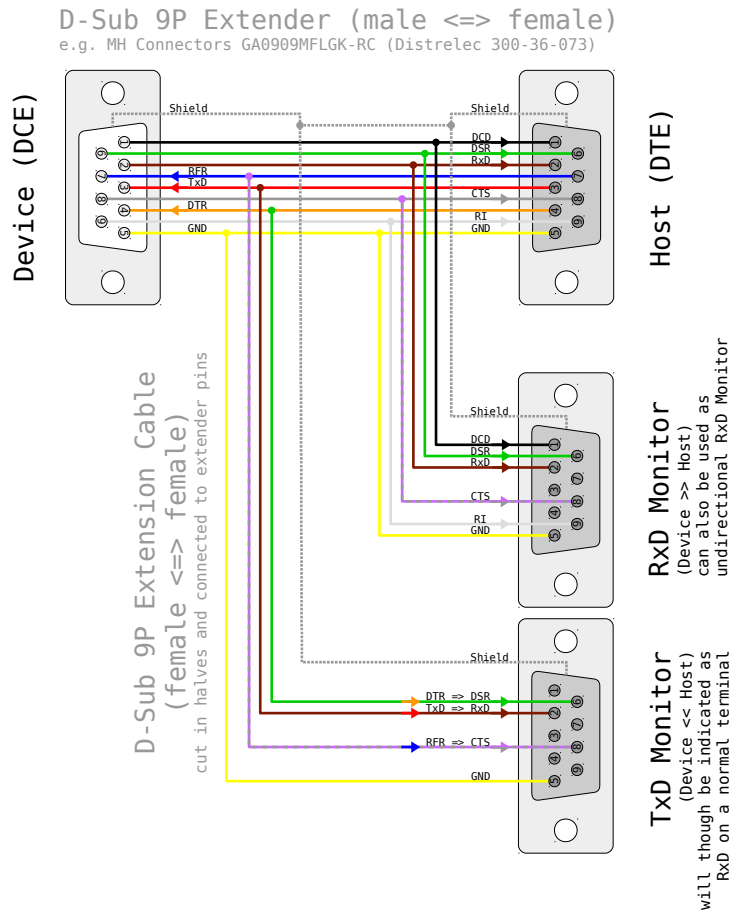


RS-232 Monitoring/Sniffing/Spying Cable

Bidirectional Full Duplex incl. Control Lines



Other Variants


- > Bidirectional Full Duplex incl. Control Lines and Data Injection
- > Bidirectional Half Duplex incl. Control Lines and Data Injection
- > Bidirectional Half Duplex incl. Control Lines

Requires a bunch of diodes and resistors. For input, see:


- > <https://www.lammertbies.nl/comm/cable/RS-232-spy-monitor.html>
- > <http://www.compuphase.com/electronics/rs232split.htm>
- > <https://www-user.tu-chemnitz.de/~heha/basteln/PC/serspy/>

Assembly


1. Preparation

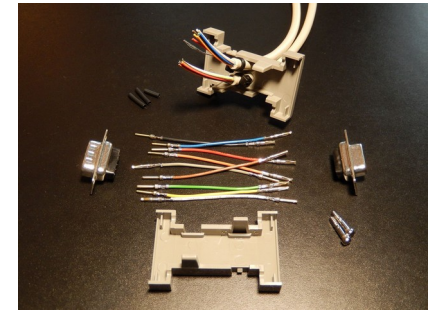


2. Connect RxD monitor cable

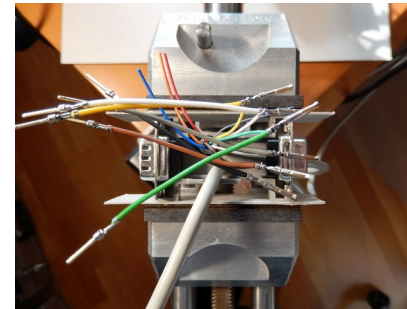

3. Connect TxD monitor cable

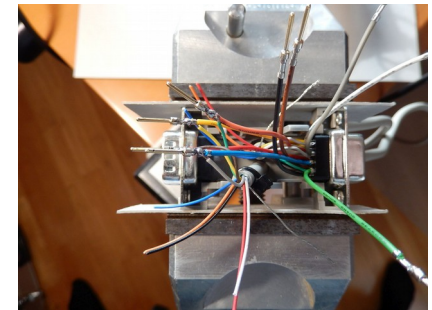

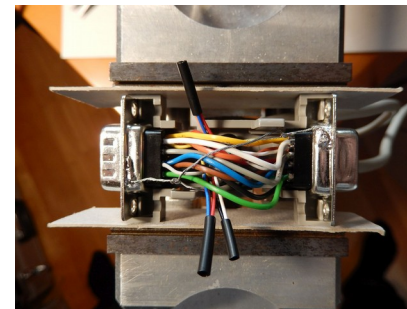4. Connect shield Insulate remaining cables



5. Finalize Done :-)

